



Finally, the lengths can be inferred from the phase of the reflection coefficients

$$\frac{-\Gamma_L}{-\Gamma_A} = \exp[j(\psi - \psi')] = \exp(j2\beta d) \quad \frac{1}{-\Gamma'_S} = \exp[j(2\pi - \phi)] = \exp(j2\beta l)$$

where  $\beta$  is the phase constant of the lossless transmission line sections.

### 1. Single shorted stub impedance matching circuit design

Write a function that calculates the lengths  $l$  and  $d$  for the single shorted stub (reporting the solution with shortest length  $d$ ) given the normalized load impedance  $z_L = Z_L / Z_0$  and the phase constant  $\beta$ ,

```
[ l, d ] = shortedstubdesign(zL,beta)
```

You are free to design the flow your function however you wish. An example flow is as follows:

1. Calculate the normalized load admittance  $y_L$ .
2. Calculate the negative reflection coefficient for the load  $-\Gamma_L$ . It might be useful to work directly with the negative reflection coefficient, denoting it with a variable `nGammaL`.
3. Calculate the angle  $\psi$  of the reflection coefficient.
4. Calculate the angle  $\psi'$  of the rotated reflection coefficient. Choose the value of  $\psi'$  that minimizes  $\psi - \psi'$ .
5. Calculate the length  $d$ .
6. Calculate the rotated negative reflection coefficient  $-\Gamma'_A$  corresponding to the selected  $\psi'$ .
7. Calculate the admittance  $y_A$ .
8. Calculate the shorted stub negative rotated reflection coefficient  $-\Gamma'_S$ .
9. Calculate the angle  $\phi$ .
10. Calculate the length  $l$ .

You may find it useful to use the *modulo* function to fold phase angles into the interval  $[0, 2\pi)$  using the MATLAB command `theta_new = mod(theta_old, 2*pi)`.

Test your function using a normalized load impedance  $z_L = 0.70 - j0.95$  and phase constant  $\beta = 2\pi$  rad/m. You should find  $l = 0.111$  m and  $d = 0.059$  m.

**№ 1: Show your results to the teaching assistant.**

Optional:

Can you develop a code for designing a matching circuit using a single *open-circuit* stub?

## Laboratory 5: Impedance matching with a single stub circuit - analysis

### 1. Calculating the frequency response of a single shorted stub circuit

Write a function that calculates the **reflection coefficient** for a single stub circuit with lengths  $l$  and  $d$ , normalized load impedance  $z_L$ , and phase constant  $\beta$ ,

```
[ Gamma ] = shortedstubresponse ( l , d , zL , beta )
```

You are free to design the flow your function however you wish. An example flow is as follows:

1. Calculate the load reflection coefficient  $\Gamma_L$ .
2. Calculate the rotated load reflection coefficient  $\Gamma'_L$ .
3. Calculate the admittance  $y_A$  towards the load. write equations
4. Calculate the rotated reflection coefficient  $\Gamma'_S$  for the short circuited stub.
5. Calculate the admittance  $y_S$  towards the short.
6. Calculate the total admittance  $y_{in} = y_A + y_S$ .
7. Calculate the reflection coefficient  $\Gamma$ .

Test your function using the example of the previous laboratory, with normalized load impedance  $z_L = 0.70 - j0.95$ , phase constant  $\beta = 2\pi$  rad/m and lengths  $l = 0.111$  m and  $d = 0.059$  m. You should find a reflection coefficient  $\Gamma = 0$ , corresponding to the matched condition (with possible deviation due to numerical rounding error).

**Nº 1: Show your results to the teaching assistant.**

### 2. Analyzing the frequency response of a single shorted stub circuit

Design the lengths  $l$  and  $d$  of a single shorted stub circuit for a normalized load impedance  $z_L = 0.4$ , with a lossless transmission line of phase velocity  $v_p = 2 \times 10^8$  m/s and an operating frequency  $f_0 = 1$  GHz (from which you can determine the phase constant  $\beta$ ).

Calculate the reflection coefficient  $\Gamma$  versus frequency  $f$  for your single shorted stub circuit with the lengths  $l$  and  $d$  that you have designed. Take a frequency range  $f = 1$  MHz to 2 GHz in steps of  $\Delta f = 1$  MHz. Note that the phase “constant”  $\beta$  depends upon frequency.

Plot the reflection coefficient  $\Gamma$  on a Smith chart, using the MATLAB command `s = smithplot(f, Gamma)`. Inspect your Smith chart, which is presented in the impedance mode.

Plot the magnitude of the reflection coefficient  $|\Gamma|$  versus frequency  $f$ .

Is impedance matching achieved at the design frequency  $f = 1$  GHz ?

In the low frequency limit  $f \rightarrow 0$ , what is the input impedance? Does this agree with what you expect at dc? The reflection coefficient  $\Gamma = -1$ , equivalent to that of a short circuit, at a frequency  $f > 1$  GHz. Why?

**Nº 2: Show your results to the teaching assistant.**

Repeat the exercise, and design a single shorted stub circuit for matching a load  $z_L = 0.04$ . Calculate the reflection coefficient  $\Gamma$  versus frequency  $f$ . Take a frequency range  $f = 1$  MHz to 2 GHz in steps of  $\Delta f = 1$  MHz. Plot the reflection coefficient  $\Gamma$  on a Smith chart, and the magnitude of the reflection coefficient  $|\Gamma|$  versus frequency  $f$ .

What do you notice about the frequency dependence of  $|\Gamma|$  near the design frequency as compared to the single stub circuit with  $z_L = 0.4$  ?

**No 3: Show your results to the teaching assistant.**