

## Laboratory 3 : Smith Chart

In this laboratory, we will develop several simple functions relating the load impedance  $Z_L$ , reflection coefficient  $\Gamma$  and input impedance  $Z_{in}$  for a lossless transmission line with characteristic impedance  $Z_0$ , phase constant  $\beta$  and length  $l$ .

### 1. Reflection coefficient and input impedance

Write a function that calculates the reflection coefficient  $\Gamma$  from the normalized load impedance  $z_L = Z_L / Z_0$ ,

```
[ Gamma ] = refcoeff (zL)
```

a function that calculates a rotated (phase shifted) reflection coefficient  $\Gamma'$  from the reflection coefficient  $\Gamma$  and round-trip phase  $\theta = 2\beta l$ ,

```
[ Gammarot ] = rotreffcoeff (Gamma, theta)
```

and a function that calculates the normalized input impedance  $z_{in} = Z_{in} / Z_0$  from the reflection coefficient  $\Gamma$  and round-trip phase  $\theta = 2\beta l$ ,

```
[ zin ] = inputZ (Gamma, theta)
```

as defined by the following equations,

$$\Gamma = \frac{z_L - 1}{z_L + 1} \quad \Gamma' = \Gamma \exp(-j\theta) \quad z_{in} = \frac{1 + \Gamma'}{1 - \Gamma'} = \frac{1 + \Gamma \exp(-j\theta)}{1 - \Gamma \exp(-j\theta)} \quad \theta = 2\beta l$$

Alternatively, you might wish to calculate input impedance  $z_{in}$  directly from the rotated coefficient  $\Gamma'$ . In the following, you may find it useful to recall,

$$\beta = \frac{2\pi f}{v_p}$$

For all of the calculations that follow, consider the case of a lossless transmission line with a characteristic impedance  $Z_0 = 75 \, \Omega$ , phase velocity  $v_p = 2 \times 10^8 \, \text{m/s}$ , and length  $l = 0.25 \, \text{m}$ .

Take a frequency range  $f = 1 \, \text{MHz}$  to  $300 \, \text{MHz}$  in steps of  $\Delta f = 1 \, \text{MHz}$ .

## 2. Reflection coefficient of RC, RL and RLC circuits on a Smith Chart

Consider three load impedances:

how to draw ??

- a) series RC circuit,  $Z_L = R + 1/j\omega C$ , with  $R = 75 \Omega$  and  $C = 100 \text{ pF}$  none
- b) series RL circuit,  $Z_L = R + j\omega L$ , with  $R = 75 \Omega$  and  $L = 200 \text{ nH}$  upper
- c) series RLC circuit,  $Z_L = R + 1/j\omega C + j\omega L$ , with  $R = 75 \Omega$ ,  $L = 200 \text{ nH}$  and  $C = 100 \text{ pF}$  origin
- d) parallel RLC circuit,  $Z_L = 1/(1/R + 1/j\omega L + j\omega C)$ , with  $R = 75 \Omega$ ,  $L = 200 \text{ nH}$  and  $C = 100 \text{ pF}$

Calculate the reflection coefficient  $\Gamma$  for the frequency range specified above, and plot  $\Gamma$  in the complex plane on a Smith chart for each of the load impedances. This can be conveniently done using a MATLAB command from the RFTtoolbox, `s = smithplot(f, Gamma)` where `s` is the handle for your Smith chart. You can add a title with the command `s.TitleTop = 'RC circuit'` for example. The values of  $\Gamma$  can be read explicitly by floating your cursor over the data point of interest.

Inspect your Smith charts. Notice that  $|\Gamma|$ , and the VSWR  $s$ , varies with frequency for these load impedances.

Why does the reflection coefficient  $\Gamma$  for the series RC circuit follow the  $r = 1$  locus in the lower half plane?

Why does the reflection coefficient  $\Gamma$  for the series RL circuit follow the  $r = 1$  locus in the upper half plane?

Why does the reflection coefficient  $\Gamma$  for the series RLC circuit follow the  $r = 1$  locus?

At what frequency  $f$  is the series RLC circuit impedance matched,  $\Gamma = 0$ , with the transmission line? What is the reactive component of the load impedance,  $x_L = \text{Re}\{Z_L\}$ , when the impedance matching condition is satisfied?

**No 1: Show your results to the teaching assistant.**

Optional: Why does the reflection coefficient  $\Gamma$  for the parallel RLC circuit follow the locus of constant normalized conductance,  $g = \text{Re}\{Z_0/Z_L\} = 1$ .

## 3. Reflection and input impedance of transmission line with a resistive load

Consider a resistive load impedance  $Z_L = 15 \Omega$ . Calculate the reflection coefficient  $\Gamma$ , the rotated reflection coefficient  $\Gamma'$  and the normalized input impedance  $z_{in}$  for the frequency range specified above.

Plot the rotated reflection coefficient  $\Gamma'$  in the complex plane on a Smith chart, using for example the MATLAB command `s = smithplot(f, Gammarot)`. Plot the real and imaginary parts of the normalized input impedance  $z_{in}$  versus frequency. This can be done simply using `h = plot(f, real(zin), f, imag(zin))` for example.

plot ???

Inspect your Smith chart and your impedance versus frequency plots.

Where on your Smith chart are the points corresponding to low frequency operation ( $f = 1 \text{ MHz}$ ) and high frequency operation ( $f = 300 \text{ MHz}$ )?

At what frequency is the transmission line acting as a  $1/4$  wave transformer?

Use your Smith chart to determine the length of the transmission line in terms of wavelengths at  $f = 300 \text{ MHz}$ , by determining the rotation angle  $\theta = 2\beta l$  at  $f = 300 \text{ MHz}$ , and then calculating  $l/\lambda(300 \text{ MHz}) = \beta l/2\pi = \theta/4\pi$ . Does this agree with direct calculation of  $l/\lambda(300 \text{ MHz}) = l \times 300 \text{ MHz} / v_p$ ?

Use your Smith chart to determine the VSWR.

**No 2: Show your results to the teaching assistant.**

**4. Reflection and input impedance of transmission line with an inductive load**

Consider an inductive load impedance  $Z_L = j\omega L$  with  $L = 20$  nH. Calculate the reflection coefficient  $\Gamma$ , the rotated reflection coefficient  $\Gamma'$  and the normalized input impedance  $z_{in}$  for the frequency range specified above.

Plot the rotated reflection coefficient  $\Gamma'$  in the complex plane on a Smith chart. Plot the real and imaginary parts of the normalized input impedance  $z_{in}$  versus frequency. Restrict your impedance figure axes to normalized impedance components within the range  $\pm 15$ .

What is the minimum frequency  $f$  required to achieve a capacitive ( $x_{in} < 0$ ) input impedance  $z_{in}$ ?

Will increasing the inductance  $L$  increase, or decrease, the minimum frequency  $f$  required to achieve a capacitive ( $x_{in} < 0$ ) input impedance  $z_{in}$ ?

**№ 3: Show your results to the teaching assistant.**

**5. Reflection and input impedance of transmission line with a series RLC circuit**

Consider a load impedance  $Z_L = R + j\omega L + 1/j\omega C$  of a series combination of resistance  $R = 75 \Omega$ , inductance  $L = 200$  nH and capacitance  $C = 100$  pF (as in exercise 2 c). Calculate the reflection coefficient  $\Gamma$ , the rotated reflection coefficient  $\Gamma'$  and the normalized input impedance  $z_{in}$  for the frequency range specified above.

Plot the rotated reflection coefficient  $\Gamma'$  in the complex plane on a Smith chart. The result is non-trivial. Plot the real and imaginary parts of the normalized input impedance  $z_{in}$  versus frequency. Restrict your figure axes to impedance components within the range  $\pm 15$ .

Inspect your Smith chart and your impedance versus frequency plots, and consider the following questions.

At what frequency  $f$  is the impedance matching condition  $\Gamma = 0$  satisfied?

Does the length  $l$  of the transmission line affect the frequency at which  $\Gamma = 0$  is achieved?

Why does  $|\Gamma| \approx 1$  in the low-frequency ( $f = 1$  MHz) and high-frequency ( $f = 300$  MHz) limits?

**№ 4: Show your results to the teaching assistant.**

Optional: Compare the Smith charts of the series RLC circuit reflection coefficient  $\Gamma$  (exercise 2c) and rotated reflection coefficient  $\Gamma'$ . Using the two charts, determine the length of the transmission line in terms of wavelengths at  $f = 300$  MHz. In other words, determine the ratio  $l/\lambda(300 \text{ MHz})$ . Confirm that your answer is the same as in exercise 3, as it must be, because the transmission line is unchanged.